

IITB - Proc CPU Design


190050096 - 190050101 - 190050103 - 190050116

Sunday 23rd May, 2021

IITB-Proc: a multi-cycle processor

Note: We faced difficulties for $2^{16} * 16$ because devices installed in quartus doesn't have dedicated ram. So, TA suggested me to reduce ram size because of few instructions. So I use 2047 downto 0 of 15 downto 0 in my project.


§1. Register file

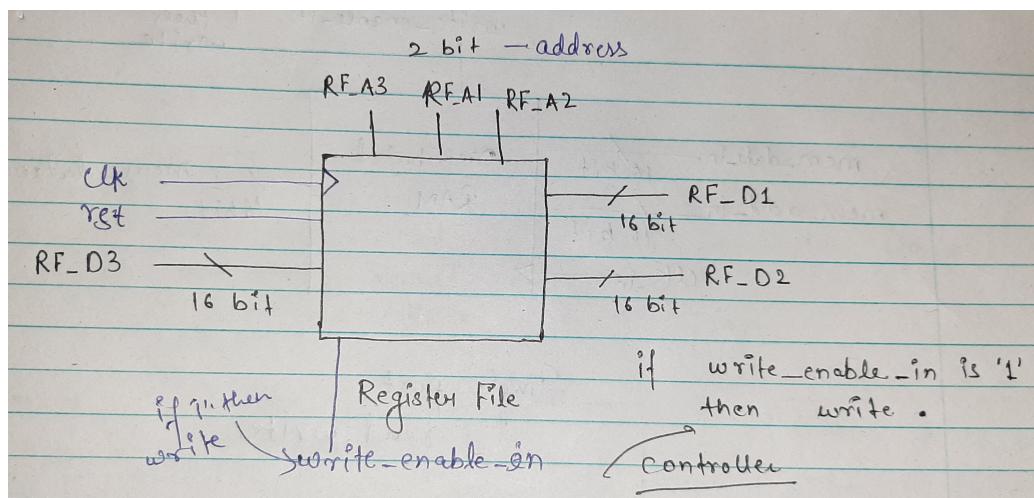

The register file consists of eight 16-bit registers. The RF stores the data provided at the port RF_D3 into location provided at port RF_A3, at every rising edge of clock cycle.


The read operation has been implemented as a combinational logic and write operation is implemented as behavioral logic using process statements.

§2. Arithmetic Logic Unit (ALU)

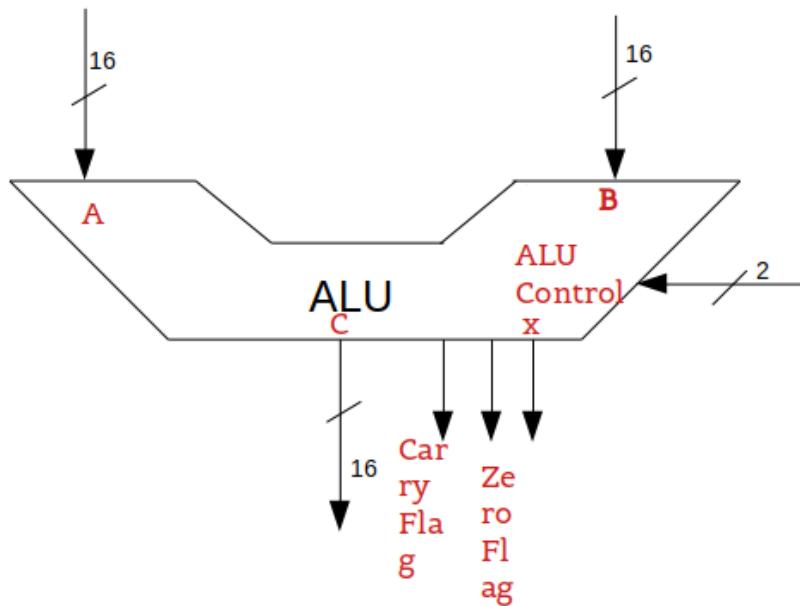

- 16 bit inputs ALU_A , ALU_B and a two bit alu_control input which determines what operation to perform and give ALU_C (16 bit output).
alu_control = "00" (addition operation), "01" (NAND operation), "10" (XOR operation)
- carry_flag_c (store carry of addition), zero_flag_z (set to 1 if $ALU_C = x"0000"$), x (1 if $ALU_C = x"0008"$) for LA/SA condition.


§3. Memory Unit

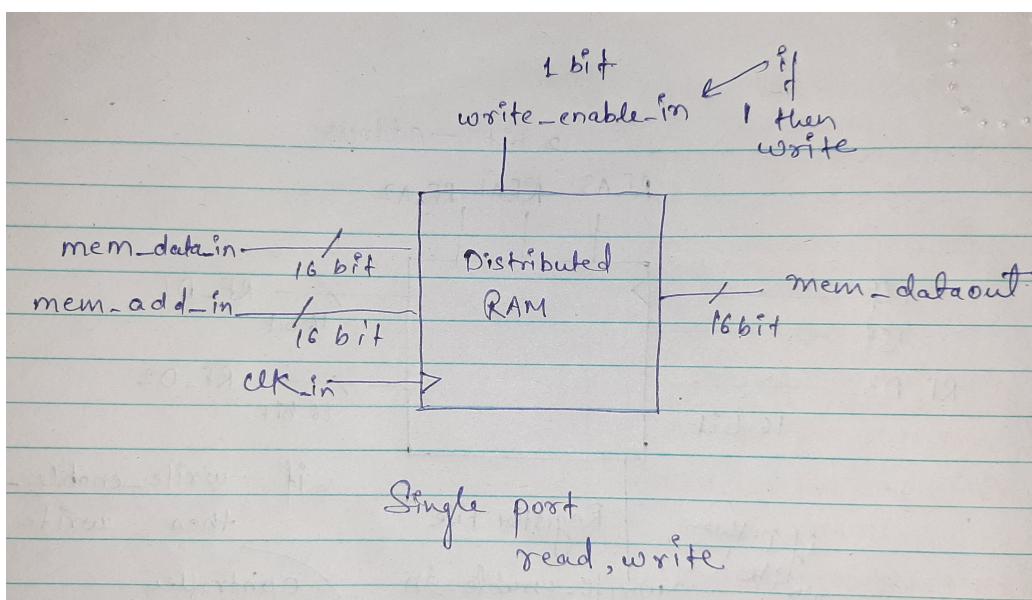


The read operation has been implemented as a combinational logic and write operation is implemented as behavioral logic using process statements.

§4. Main Unit & FSM

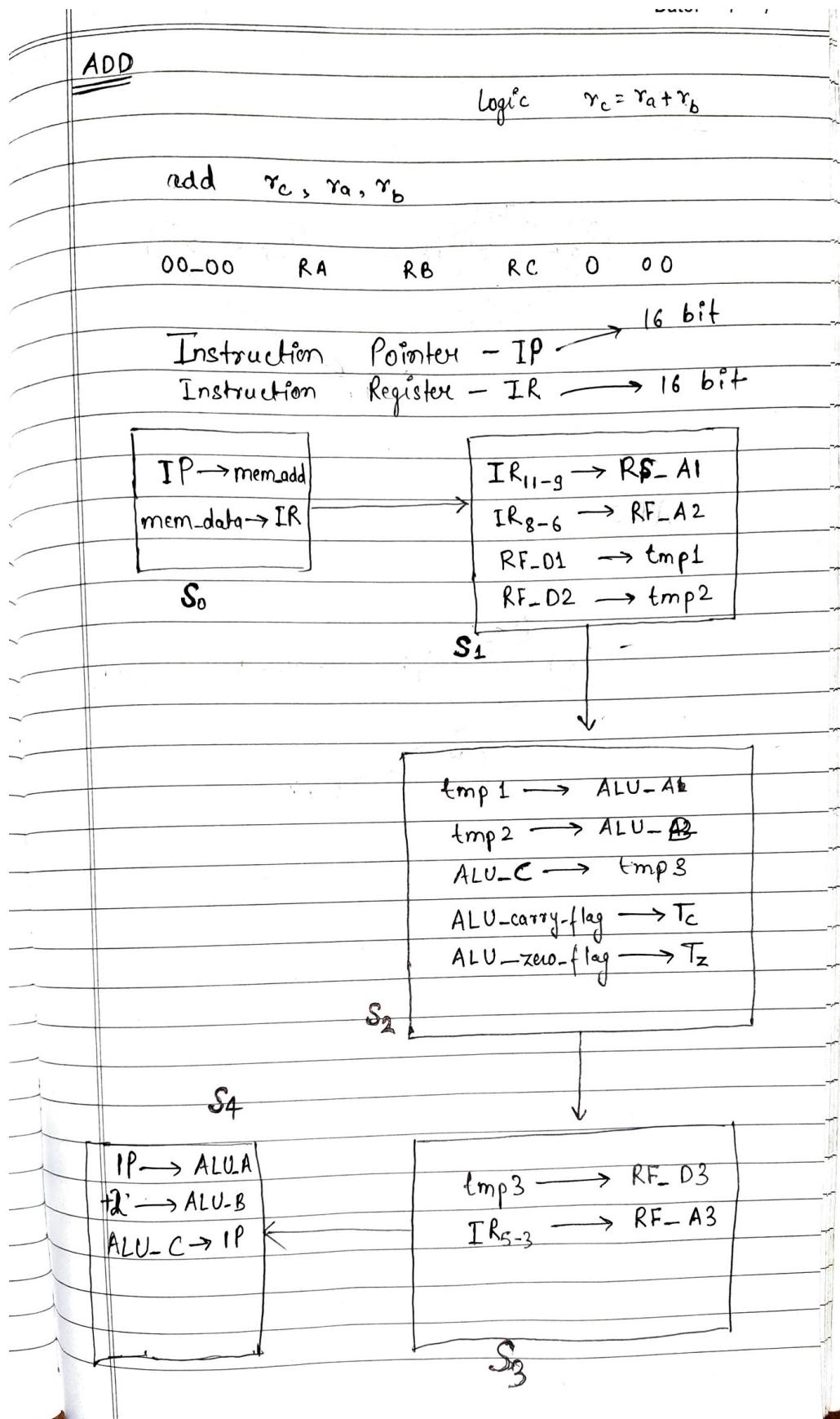We have implemented the finite statemachine in this part using behavioural VHDL logic.
FSM



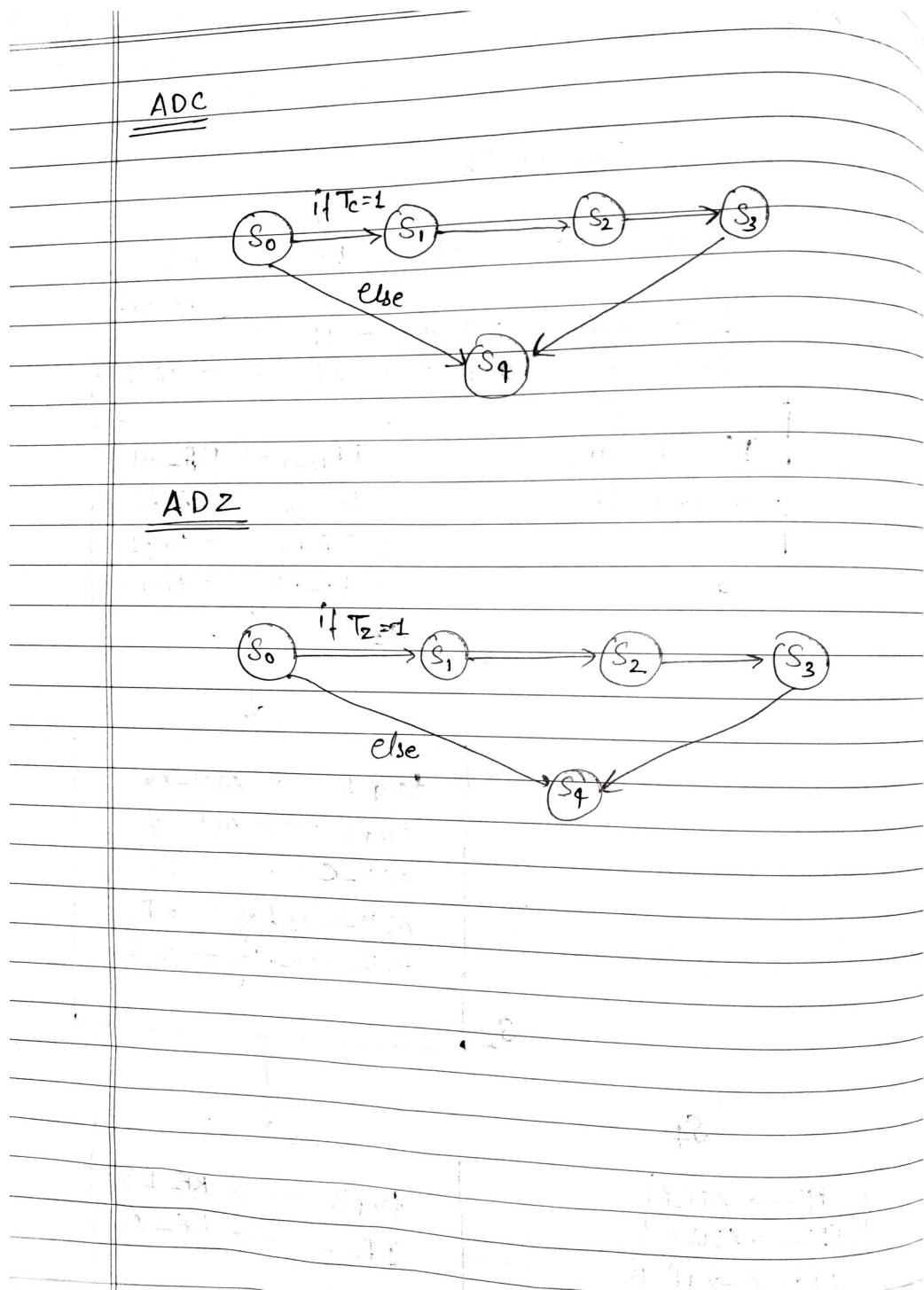

ADI






Add Intermediate (1)


00_01 RA RB 6 bit
imm
-ediate



add rb, ra, imm 6

Add content of regA with imm (sign extended)
and store result in regB.

It modifies C and Z flags

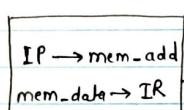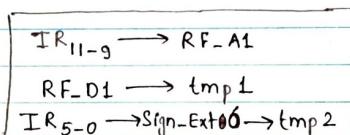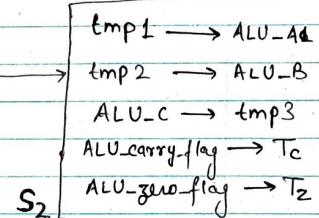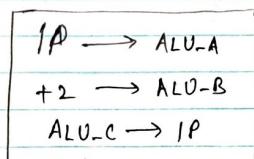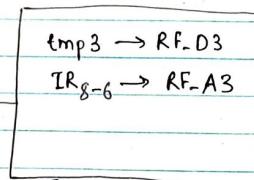S₀S₅S₂S₄S₆

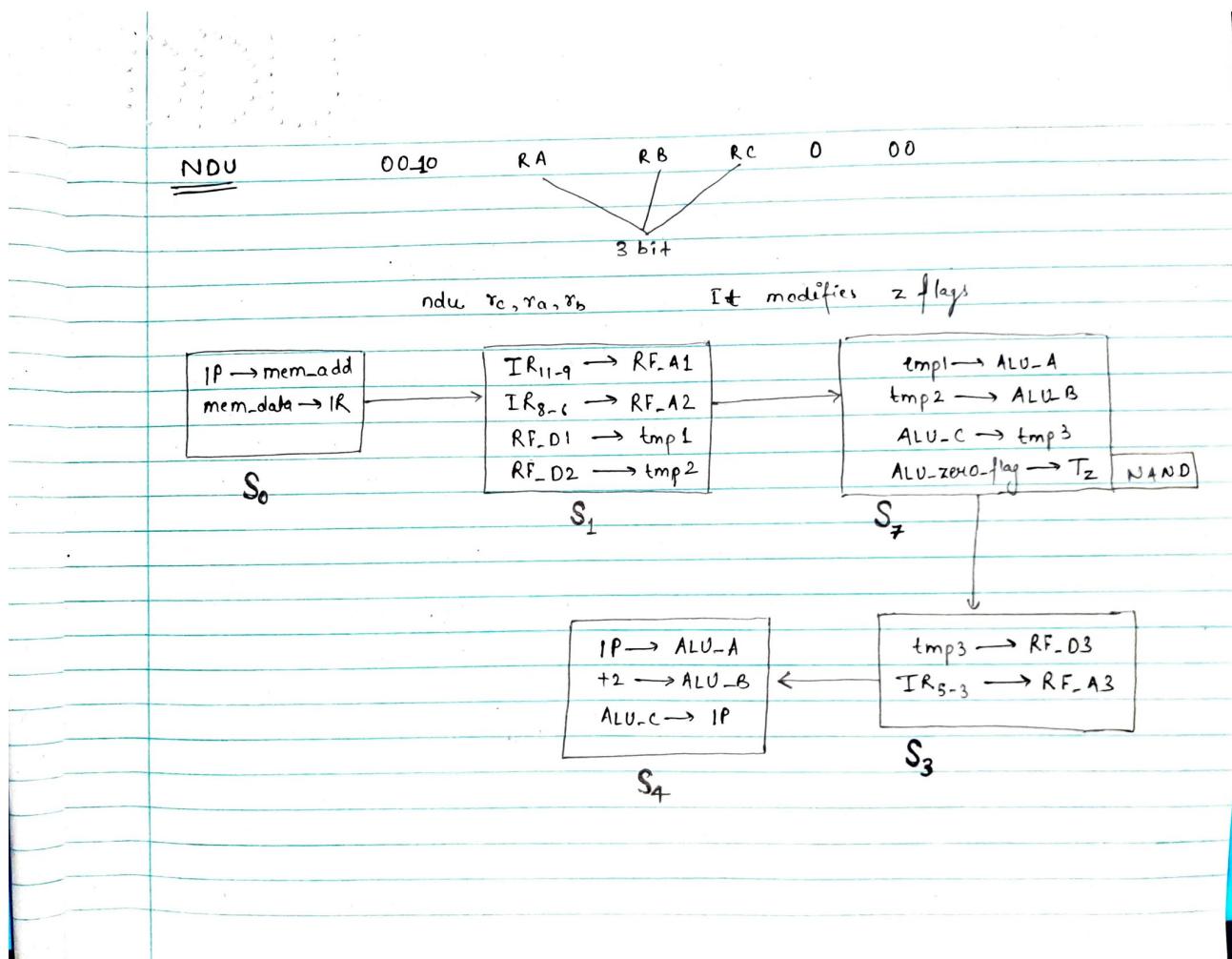

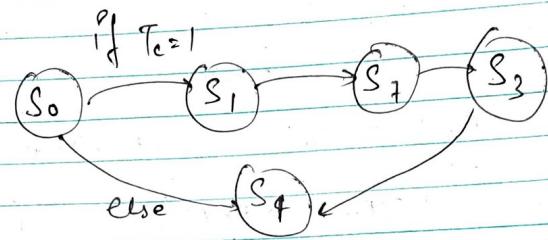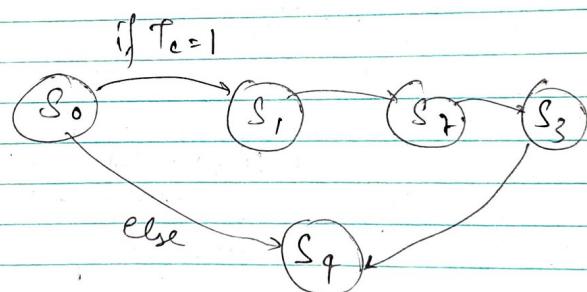
NDCNDZ

LHI 00-11 RA 9 bit Immediate
 4bit 3bit

Load Higher Immediate

lhi, ra, imm

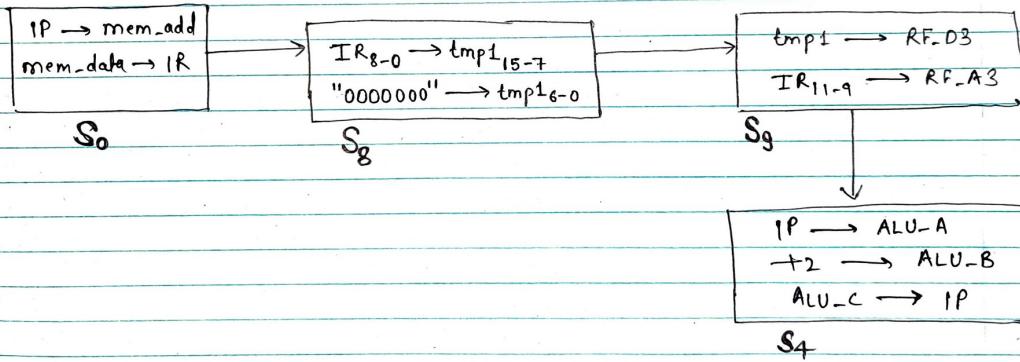Place 9 bits immediate into msb 9 bits of register A
 and lower 7 bits are assigned to zero.



LW




lw ra, rb, imm

Load


01-00 RA RB
 3 bit 6 bit immediate

Load value from memory into regA. Memory address is computed by adding immediate 6 bits with content of regB.



* It modifies a flag.

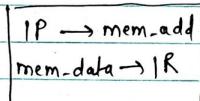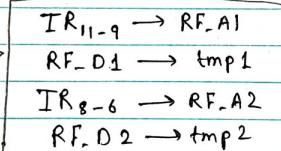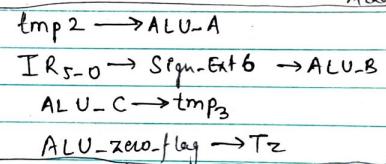 S_0  S_1  S_{10}

Update IP/PC

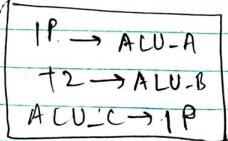 S_4

Update RF

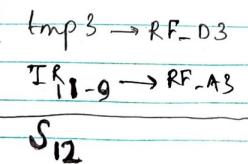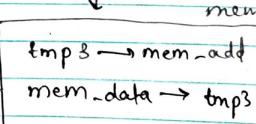 S_{12}  S_{11}

memory read

Add

SW

Store

01_01 RA RB
 3 bit






6 bit Immediate

SW ra, rb, Imm

Store value from reg A into memory.

Memory address is formed by adding immediate 6 bits with content of reg B.

Add

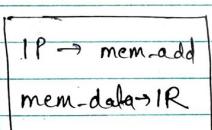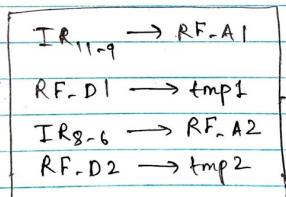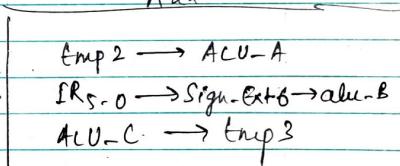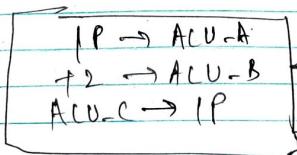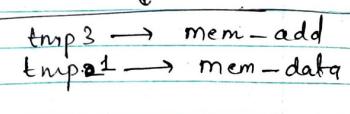
S₀S₁S₁₃S₄S₁₄


LA

15-12	11-9
01-10	RA
4 bit	3 bit

Im ra

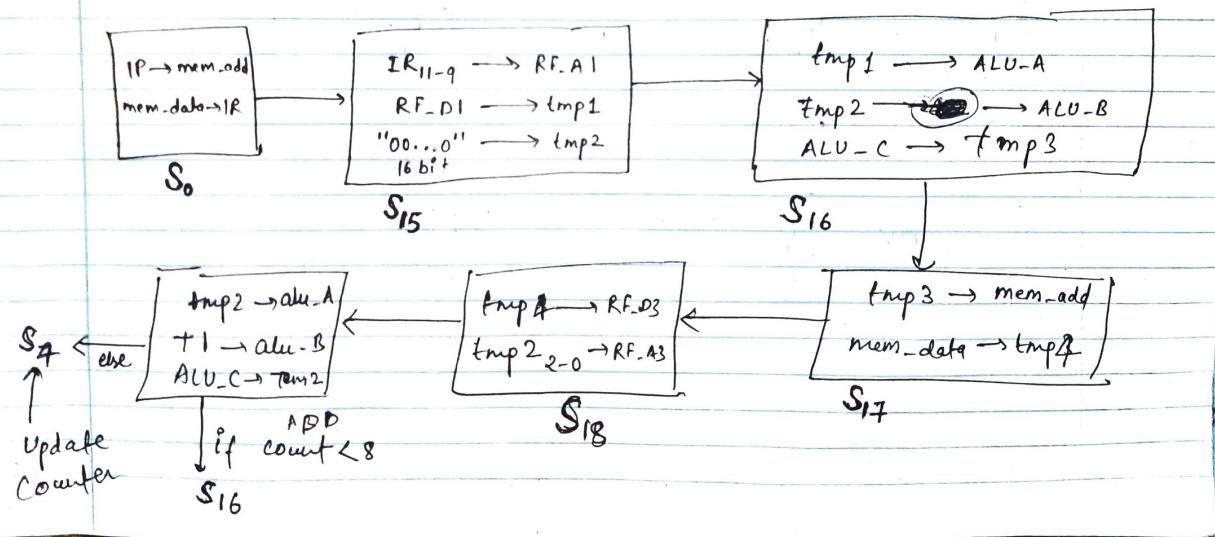Load All registers ($R_0, R_1, R_2 \rightarrow R_x$)
 Memory address is given in regA. Registers are loaded from consecutive addresses.



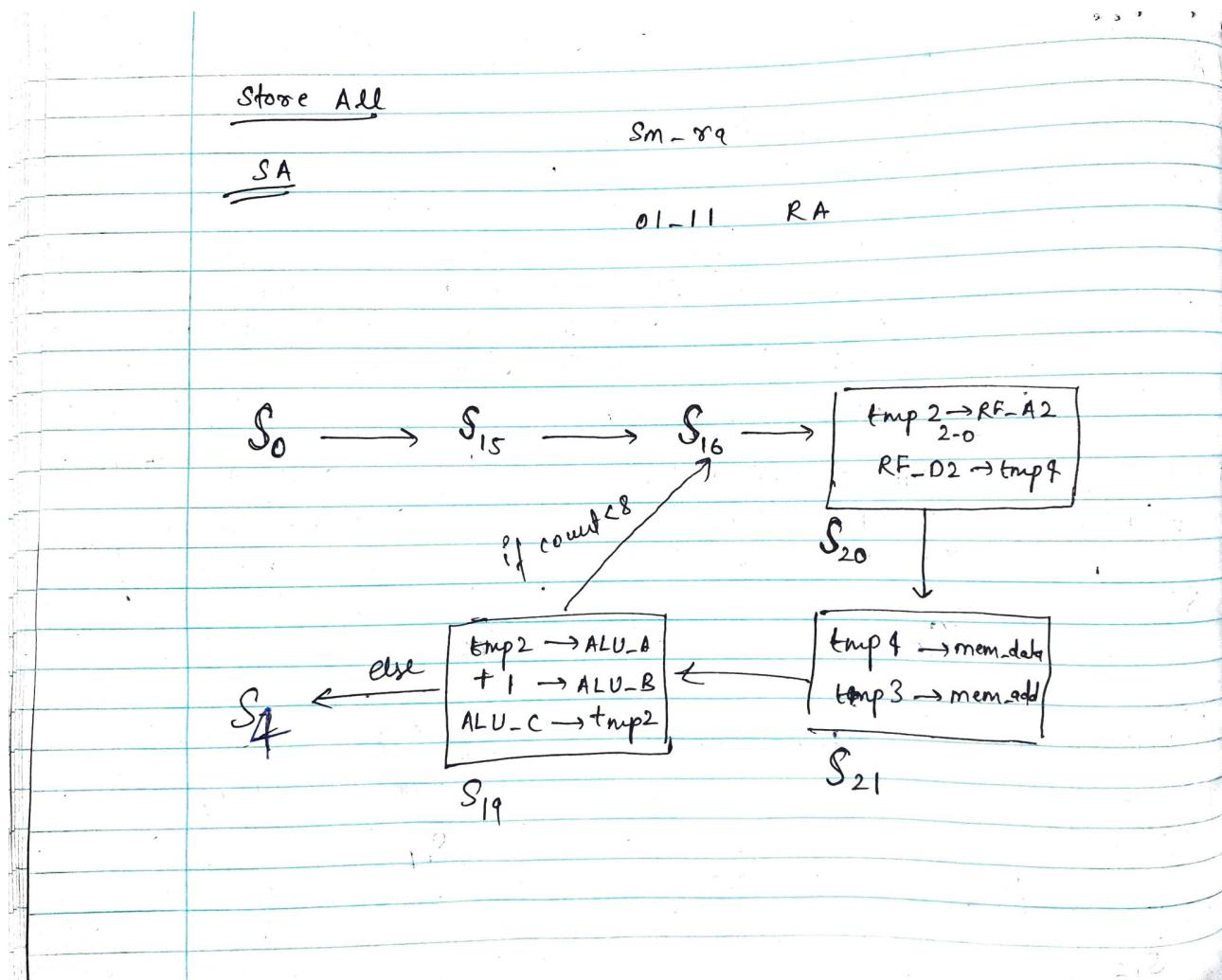

BEQ Instruction





11-00	R A	R B	6 bit immediate
15 12 11 9	8	6	5 0

Branch

On equality

beq ra,rb,imm

If content of reg A and reg B are same,
 branch to PC+imm, where PC is the address of
 (IP+imm) (IP) beq

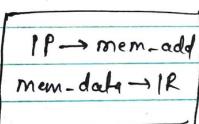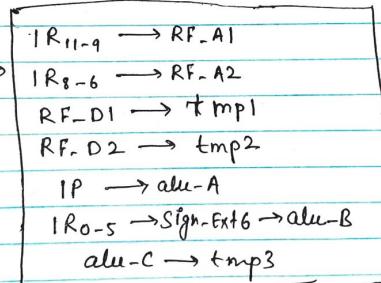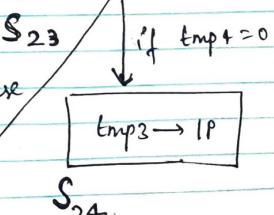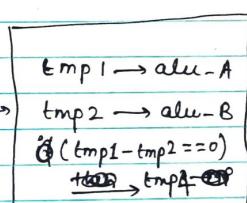S₀S₂₂S₂₃S₂₄

JAL :

10-00	RA	9 bit immediate offset
15 12 81 9 8		0

Jump and


Link

jalr, ra, imm

Branch to address IP + Imm (PC + Imm)

Store PC into regA, where PC is
(IP)

the address of jalr instruction

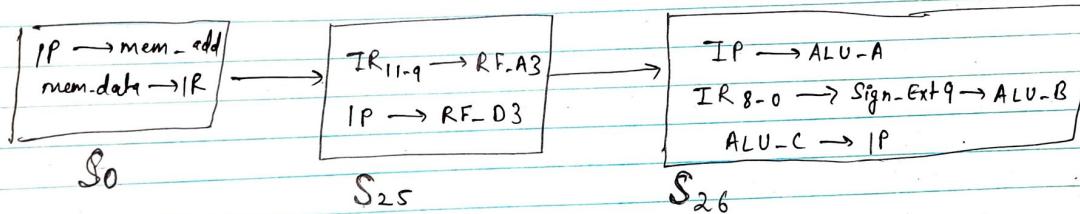

JLR :

10-01	RA	RB	000-000
15	12 11	9 8 6 5	0





Jump and Link
Register

jlr ra, rb


Branch to the address in reg B

Store PC into reg A, where PC is
(IP)

← the address of the jlr instruction.

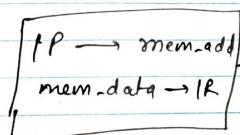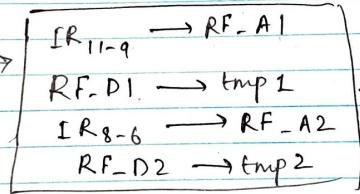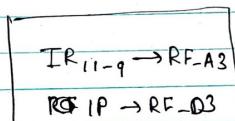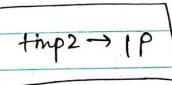S₀S₁S₂S₂₇

Circuit Diagram

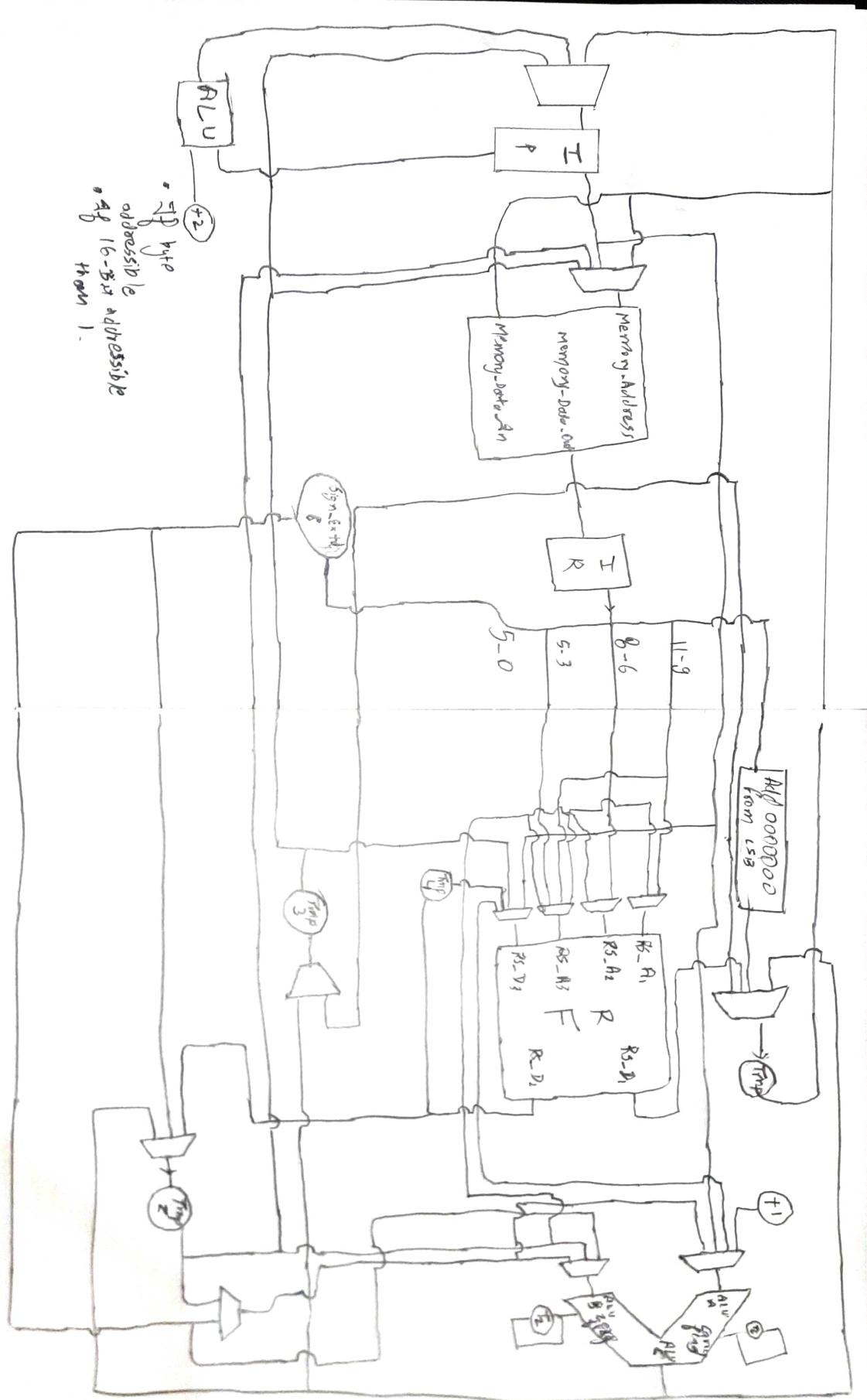


Testing of VHDL code in the Project


Testing of Component

1. SixteenbitFullAdd

a. RTL Viewer

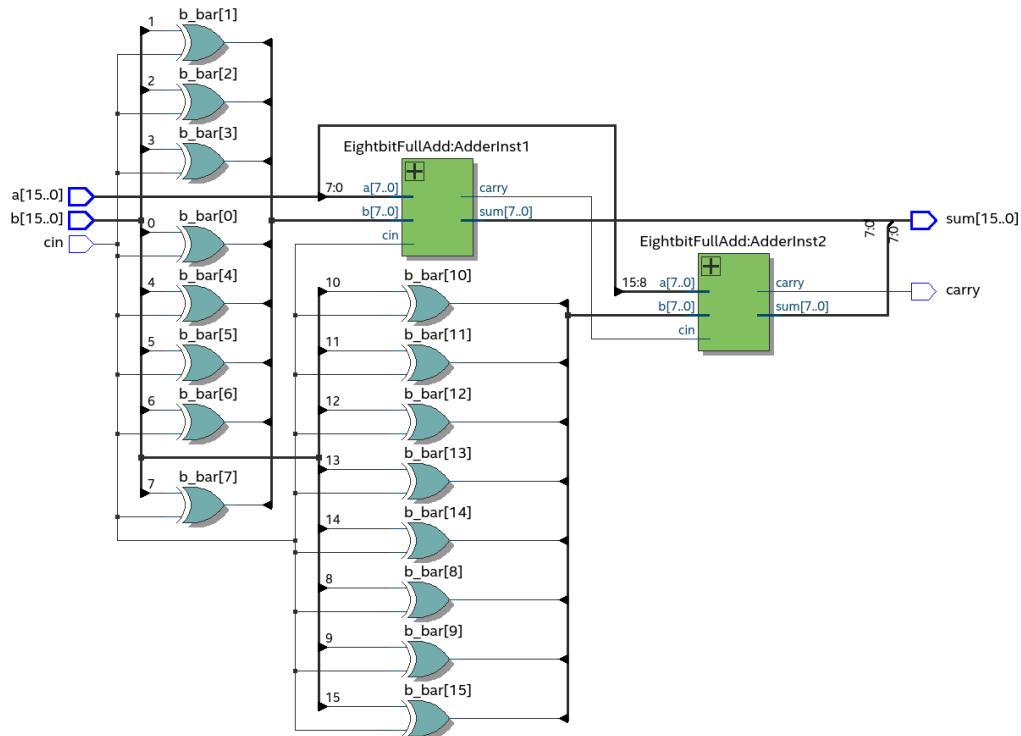

b. Waveform

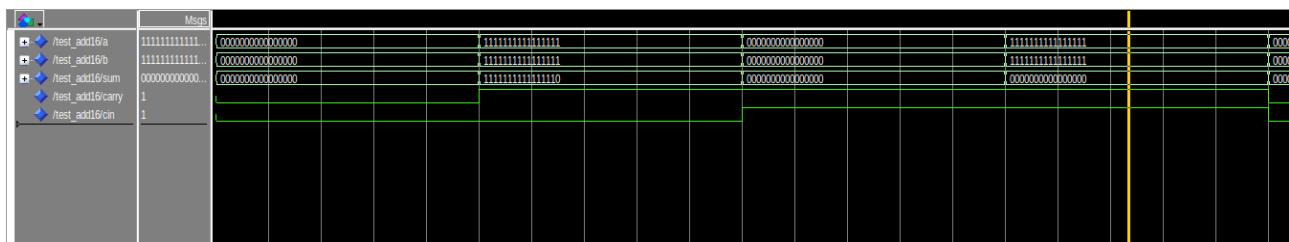


c. Testbench for SixteenbitFullAdd

TEST_ADD16.vhd

2. Register File

a. RTL Viewer

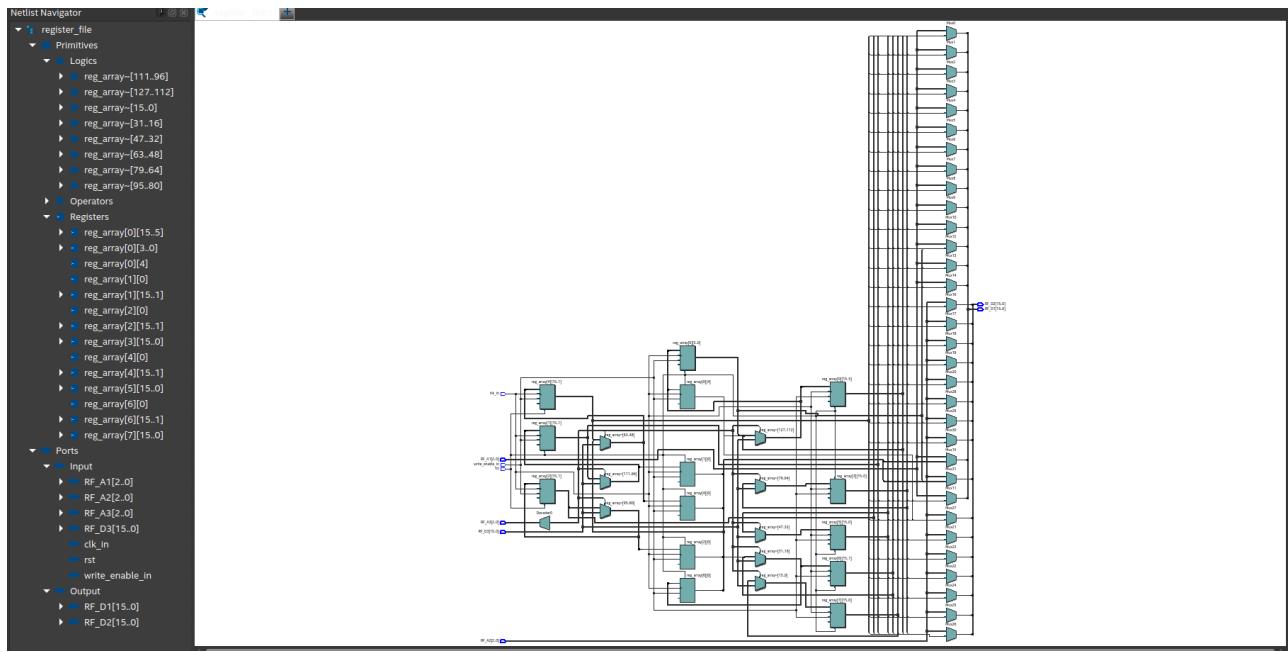


b. Waveform

First rst hold to 100 ns. When rst is high, we are storing some fixed random value in the register. Attached below.

```
if(rst = '1') then
    reg_array(0) <= x"0010";
    reg_array(1) <= x"0001";
    reg_array(2) <= x"0001";
    reg_array(3) <= x"ffff";
    reg_array(4) <= x"0001";
    reg_array(5) <= x"0000";
    reg_array(6) <= x"0001";
    reg_array(7) <= x"0000";
```

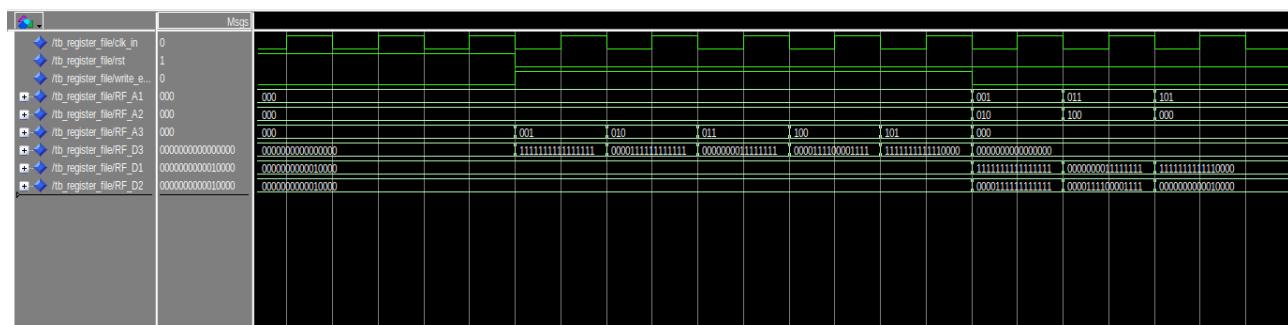After that, we write five 16bit data into register(shown in waveform) then read that to show that writing writing take place at appropriate location.




c. Testbench for SixteenbitFullAdd



tb_register_file.vhd


3. ALU

a. Diagram

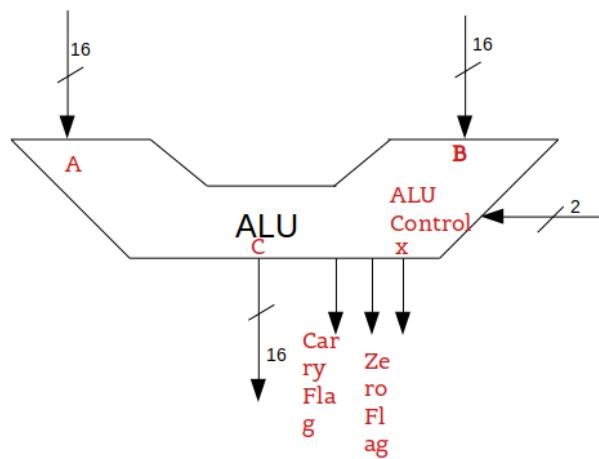


b. RTL Viewer

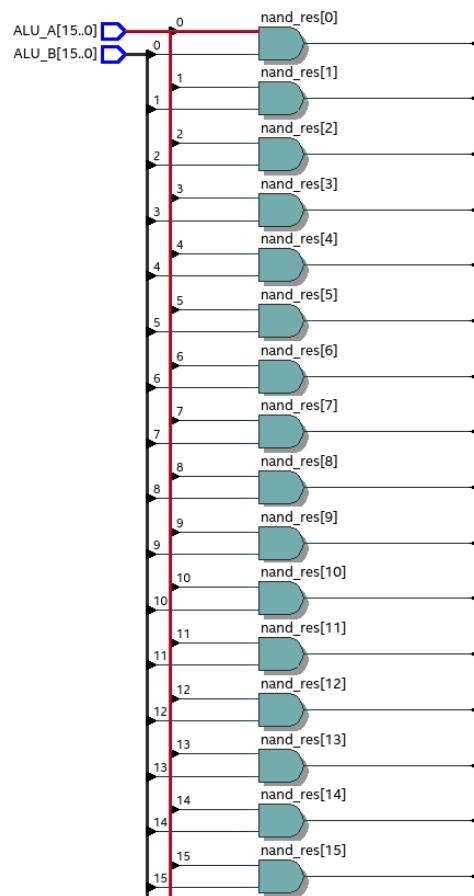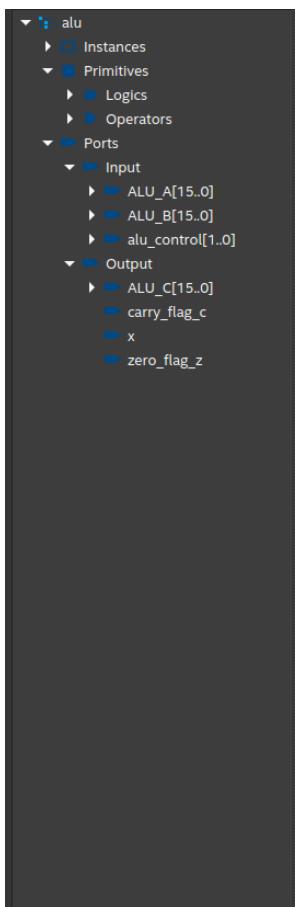

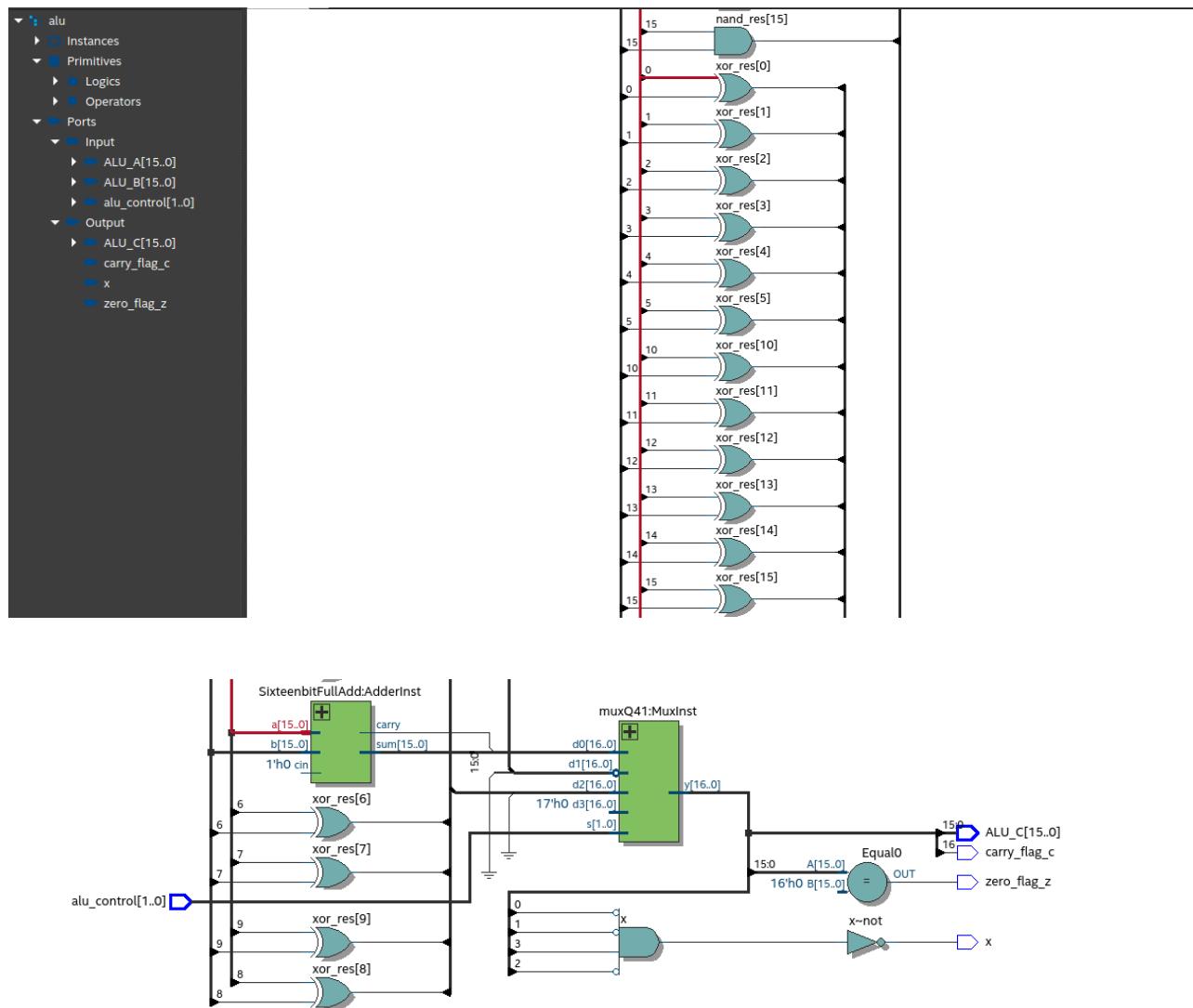

c. Waveform

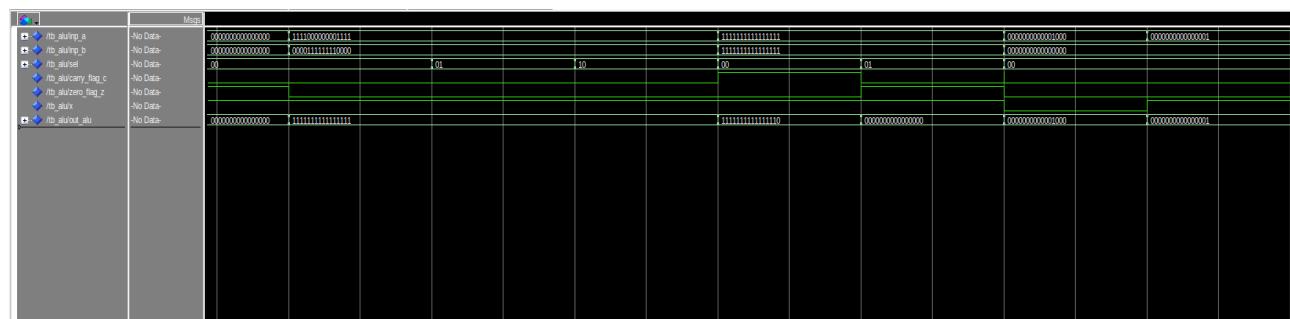


d. Testbench for ALU

tb_alu.vhd


4. Memory Async read sync write(single port) We faced difficulties for $2^{16} * 16$ because devices installed in quartus doesn't have dedicated ram. So, TA suggested me to reduce ram size because of few instructions. So I use 2047 downto 0 of 15 downto 0 in my project.

a. RTL Viewer

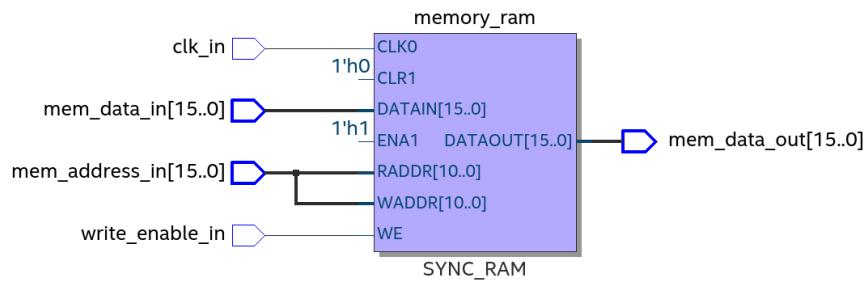


b. Waveform

– write

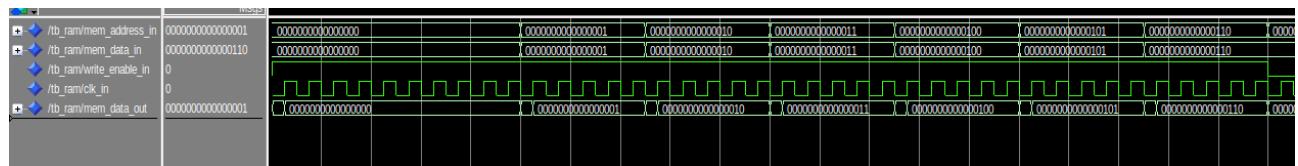

– read

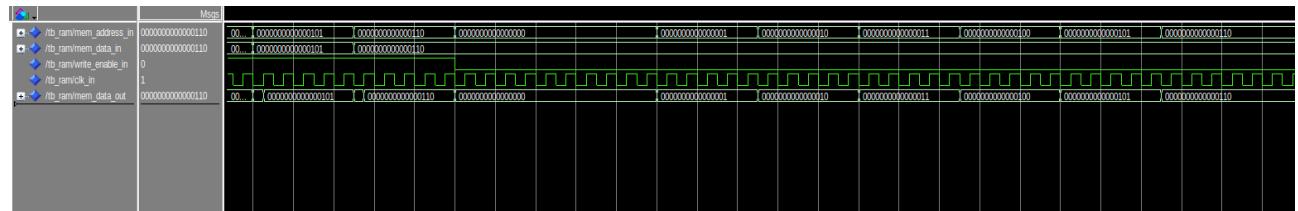


c. Testbench for memory_asyncread tb_ram.vhd

TESTING OF INSTRUCTION

Decide what are all the sequences of instructions that you want to test and keep them as initial values in the RAM. Then supply clock and reset through the test bench and test it.

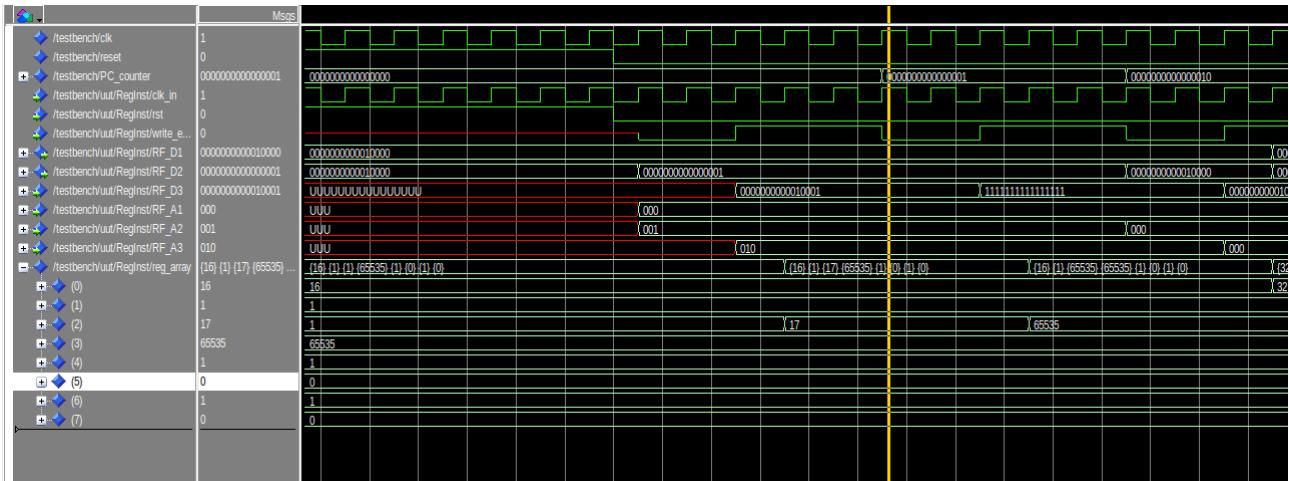1. ADD & NDU

Let $RA \leftarrow "000"$, $RB \leftarrow "001"$ and $RC \leftarrow "010"$. So, we store 0 => 0000_000_001_010_0_00 & 1 => 0010_000_001_010_0_00.




Okay, as you can see initially 16 is stored in RA, 1 is stored in RB. After add operation you can see that 17 is stored in RC and after ndu operation 65535 is stored in RC.

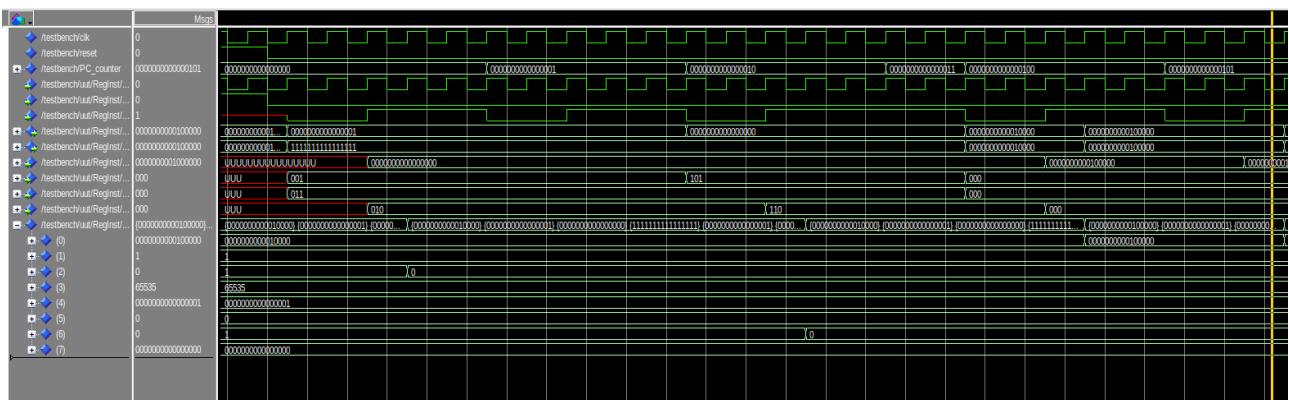2. ADD & ADC & ADZ & ADI

Let $RA \leftarrow "001"$, $RB \leftarrow "011"$ and $RC \leftarrow "010"$. So, we store 0 => 0000_001_011_010_0_00 & 1 => 0000_001_011_010_0_01.

for adi & adz, 2 => 0001_101_110_000000 (RA="101" and RB = "110"),
3 => 0000_001_011_010_0_10(RA, RB, RC defined above).



As you can see initially 1 is stored in RA, 65535 is stored in RB. After add operation you can see that 0 is stored in RC and after adc operation then still 0 is stored in RC because tc = 1 from previous add operation, After adi operation take RA index 5 and RB index 6 which make tz = 1 and then adz operation take place .


Similarly, ndc and ndz verified.

3. LHI & LW & SW

LHI

00_11 001 11111111

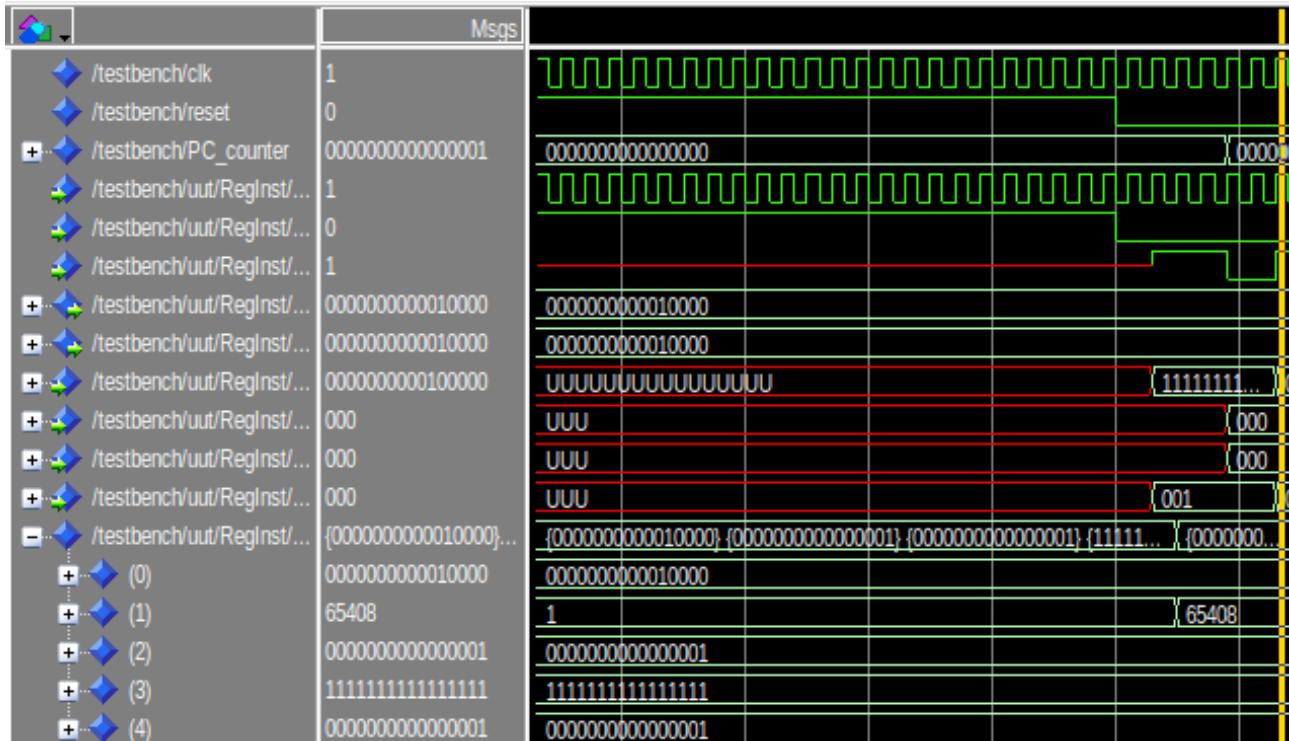After reset, "001" register RA contains value = 1 or "0000000000000001" (because we're initialising in reset operation for simplicity). After LHI operation, "001" register RA should contain 111111111_0000000 (in decimal 65,408). Let's see in the waveform.




See in the waveform value changes from 1 to 65408. I modify radix to see in decimal.

LW

01_00 000 001 000001

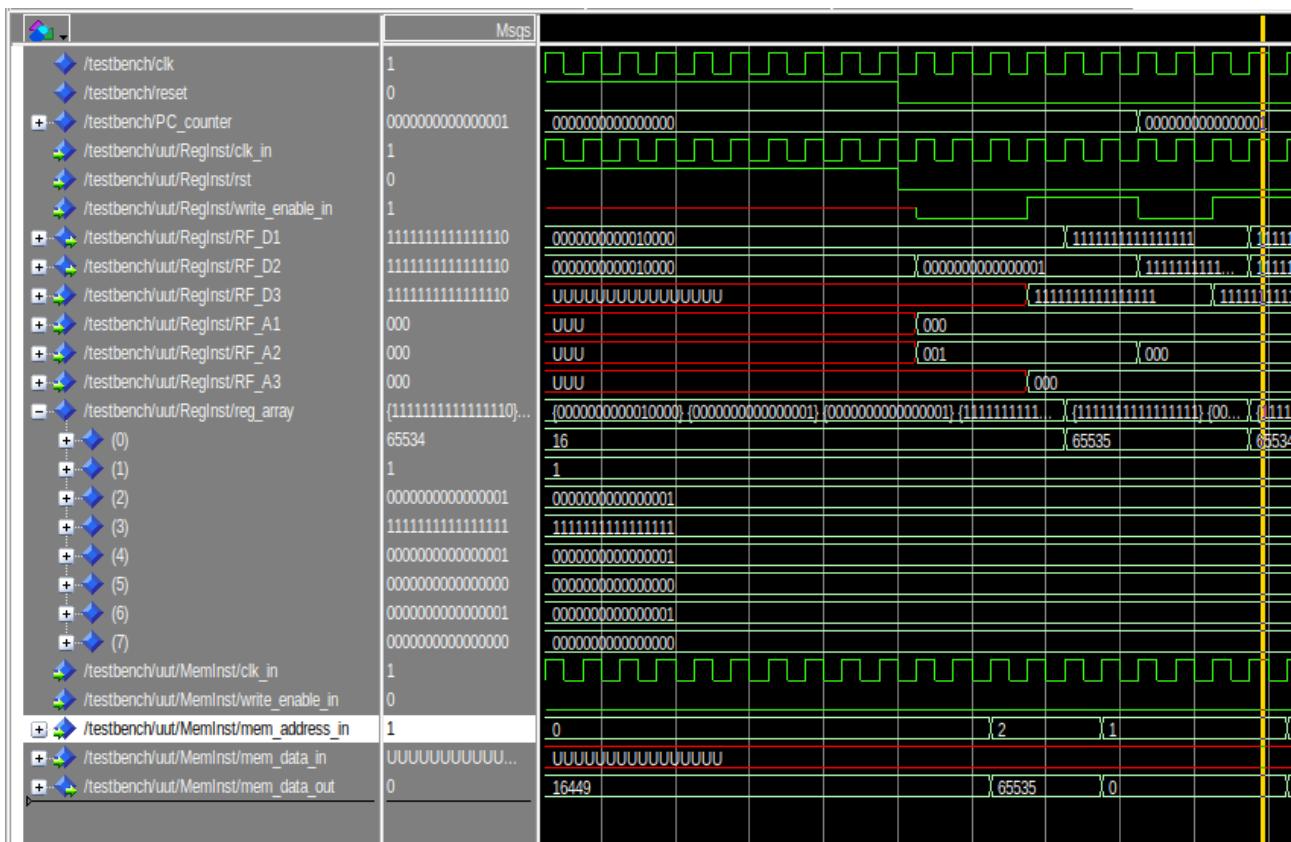RA = "000", RB = "001", because of reset content of RB is 1 (in decimal unsigned). So, memory address from this come out to be 2 (in decimal unsigned). Let's store 1111_1111_1111_1111 at memory location 2. and see indeed our register RA contain 1111_1111_1111_1111 in waveform.




See in the waveform. I modify radix to see in decimal.

SW

01_01 000 001 000001

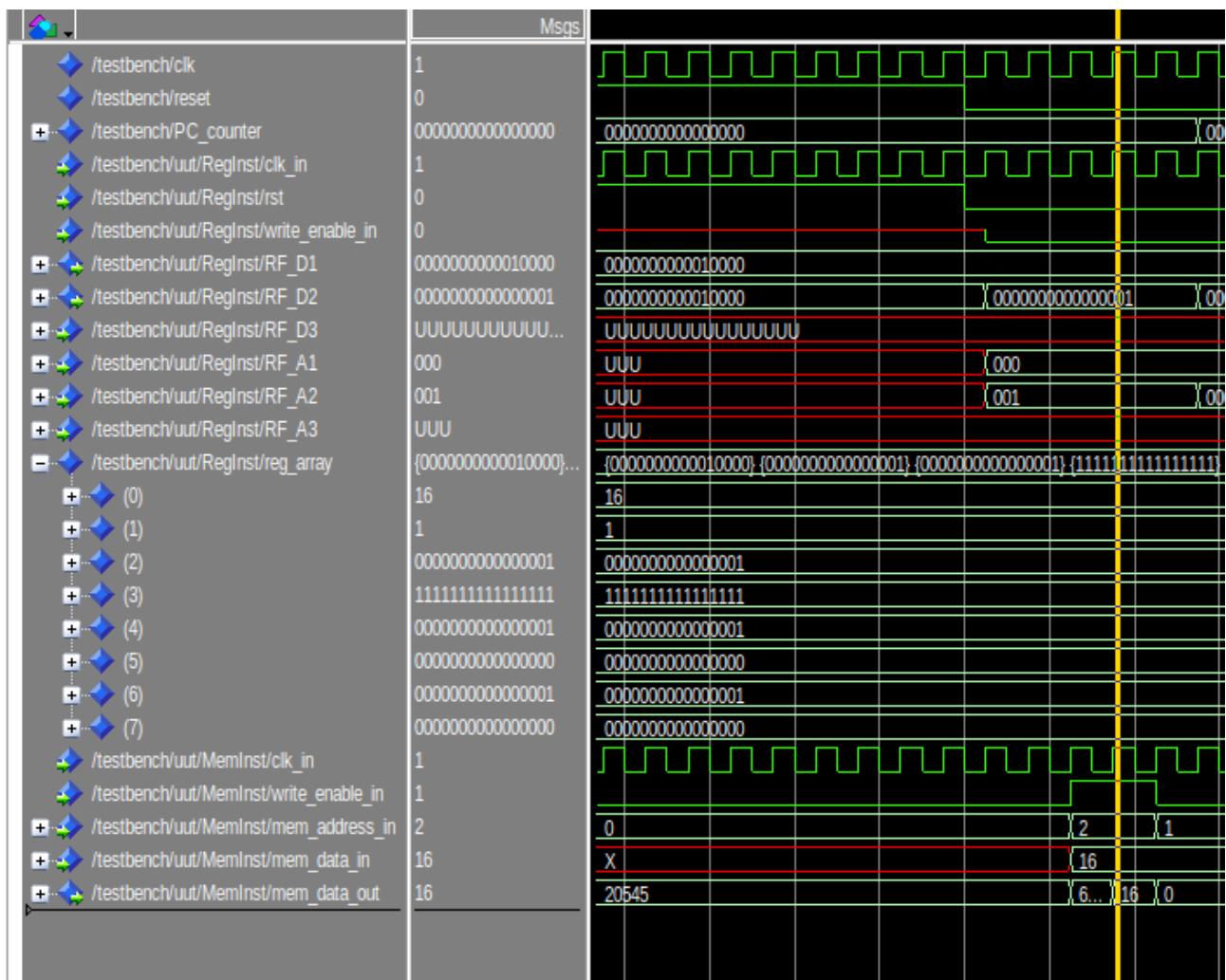RA = "000", RB = "001" , because of reset content of RB is 1 and RA is 16(in decimal unsigned). So, memory address from this come out to be 2 (in decimal unsigned). Let's store see that 16 from register RA store in memory location 2 in the waveform.




As you can see in last three line of waveform, 16 is stored in memory store at location 2. I modify radix to see in decimal.

4. LA & SA

LA

0110_001_000000000

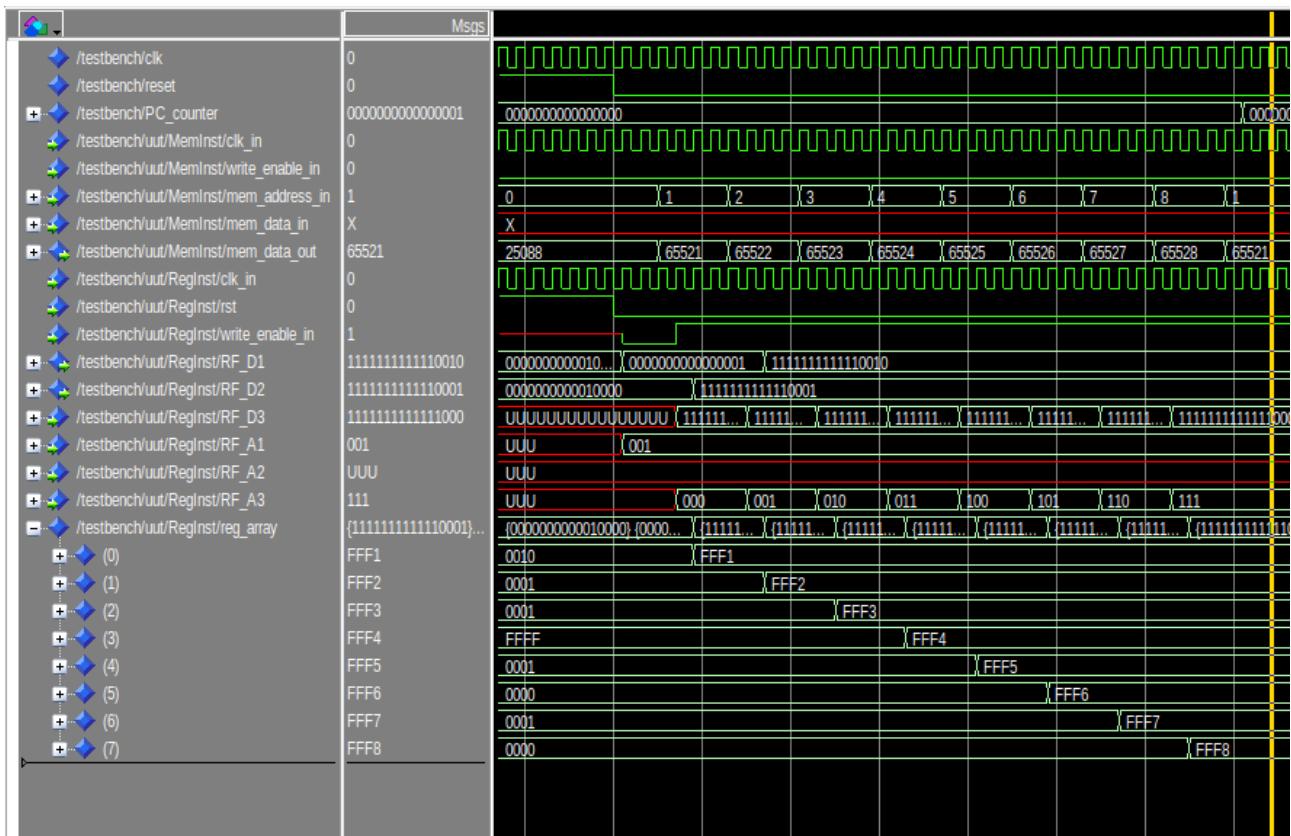RA = "001" (mem address store in RA). So, by reset 1 is store in RA. So, let's put 0 => 0110_001_00000000, 1 => x"fff1", 2 => x"fff2", 3 => x"fff3", 4 => x"fff4", 5 => x"fff5", 6 => x"fff6", 7 => x"fff7", 8 => x"fff8" in memory. Let's see our waveform what's stored in our register from R0 to R7.




Okay, so our waveform show correct result.

SA

0110_001_000000000

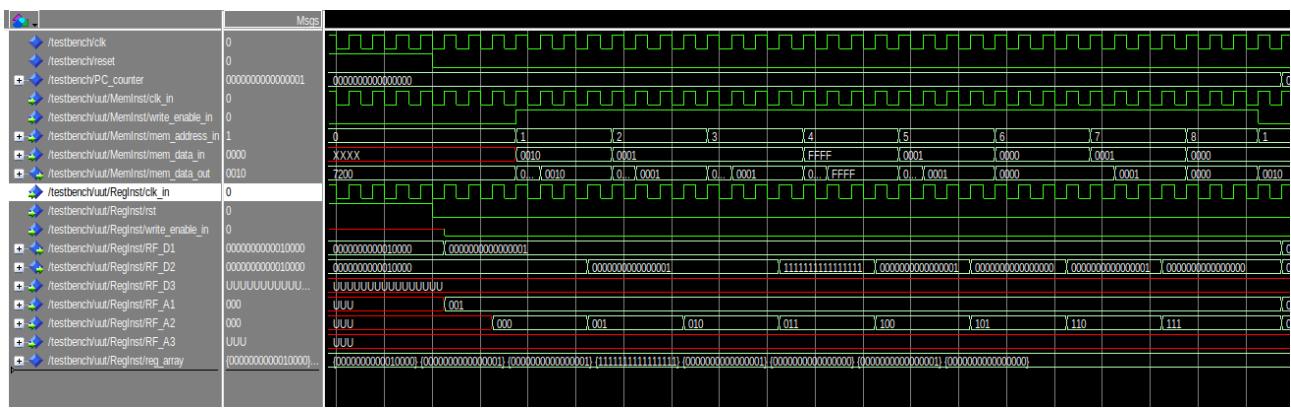RA = "001" (mem address store in RA). So, by reset 1 is store in RA. So, let's put 0 => 0110_001_000000000 in memory. Due to reset, our register from R0 to R7 have R0 <= x"0010", R1 <= x"0001", R2 <= x"0001", R3 <= x"ffff", R4 <= x"0001", R5 <= x"0000", R6 <= x"0001", R7 <= x"0000". Let's see waveform where and what data going to store in memory



Our waveform show what value is going to store in memory and which position. This clearly matches with our assumption given above.

5. BEQ & JAL & JLR


BEQ

1100 000 001 000011

Due to reset, RA = 0 (contains 8) and RB = 1 (contains 1). So, there are not equal that's why IP move to next position.

1100 001 010 000011

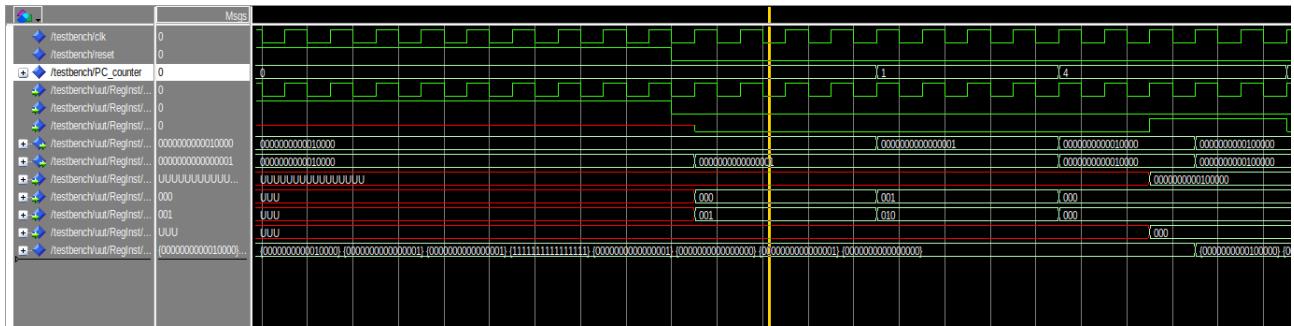Due to reset, RA = 1 (contains 1) and RB = 2 (contains 1). So, there are equal that's why IP move to IP + Imm. Let's see the waveform.



As you can see in the waveform that PC_counter move to next after first instruction then move to IP_Imm after second operation.

JAL & JLR


1000 000 0000000011

RA = 0 (contains 8 initially) and IP = IP + Imm after instruction completion.

And let's store JLR instruction in IP+Imm location

1001 001 010 000000

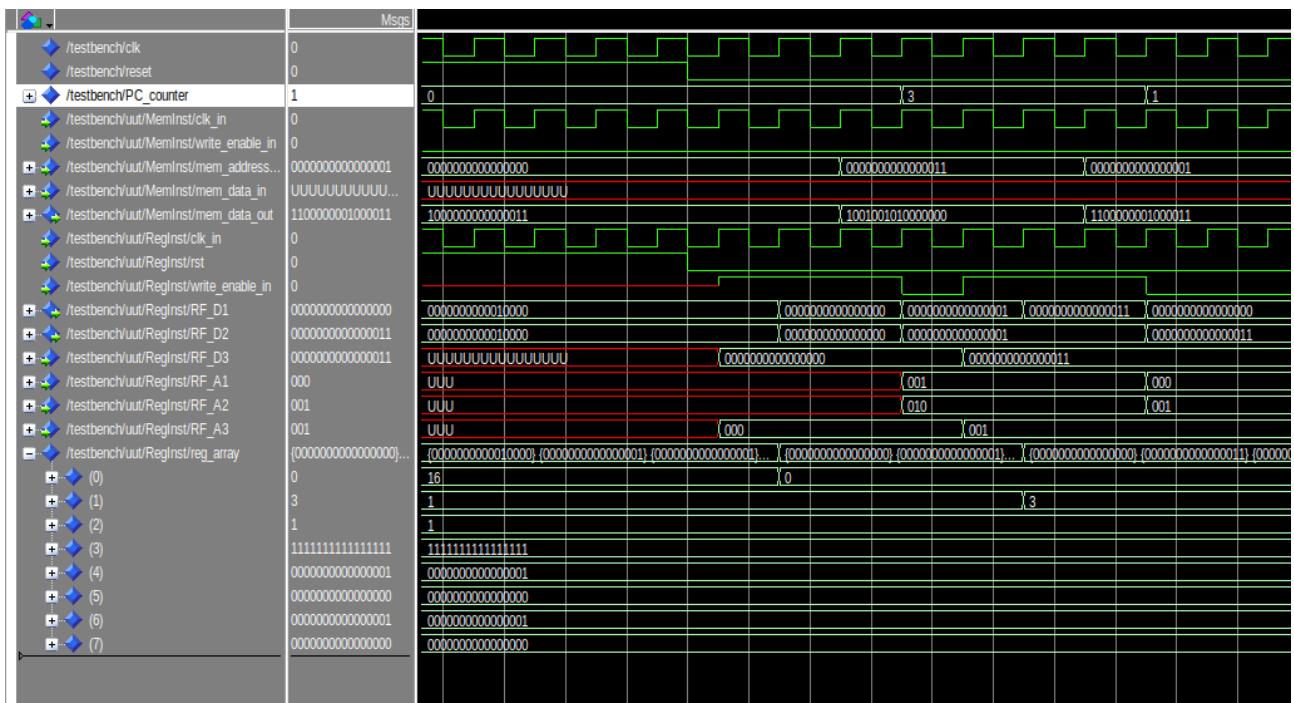RA = 1 (contains 1 initially) and RB = 2 (contains 1 initially) Lets see waveform.



As you can see in the waveform it clearly satisfies what we assume to be.

Testbench that I use is given here and all instruction is initialised in memory before use.

END
